
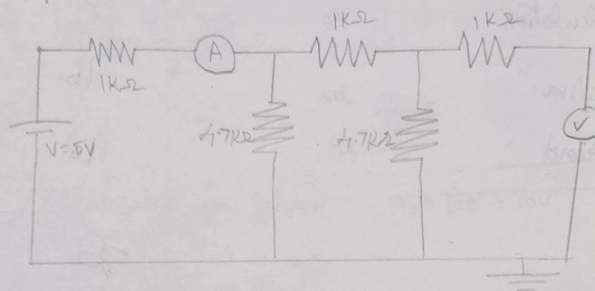


i) Output open circuit

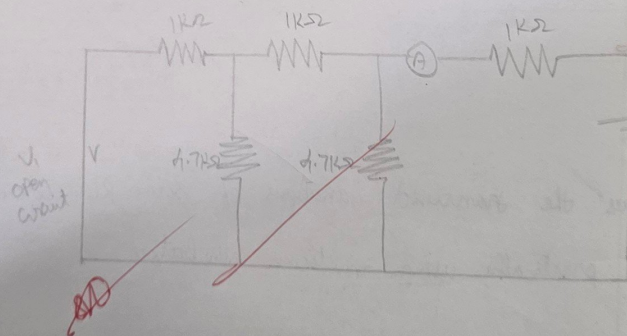

ii) Input open circuit



269
13/16

Aim:

To
using m

Apparatus

S
No

1
2
3
4
5
6

Procedure

- * Connect board
- * First O/P
- * Secondly O/P

Lab 9
13/12/20

EXPERIMENTAL DETERMINATION OF Z PARAMETERS

Aim:

To calculate and verify Z parameters of a two port network using multisim simulator

Apparatus required:

S No	Component	Specification	Qty
1.	Power supply	-	1
2.	Multimeter	-	1
3.	Resistor	10K Ω ,	
4.	Bread board	-	1
5.	wires	-	-
6.	PC with multisim simulator	-	-

Procedure:

- * Connect the circuit as shown in figure, switch on the experimental board
- * First open the o/p terminal supply or to I/P terminal. Measure the O/P terminal voltage and I/P current
- * Secondly, open I/P terminal as supply to o/p terminal. Measure I/P voltage O/P current

Observation:

S.No	Output open circuit ($I_2=0$)			$Z_{21} = V_2/I_1 (\Omega)$	$Z_{11} = V_1/I_1 (\Omega)$
	V_1	V_2	I_1		
1.	5	2.6	2.1	1.23 K Ω	2.38 K Ω
2.	5	2.55	2.03	1.22 K Ω	2.40 K Ω
3.	5	2.63	2.12	1.22 K Ω	2.33 K Ω

S.No	Input open circuit ($I_1=0$)			$Z_{12} = V_1/I_2 (\Omega)$	$Z_{22} = V_2/I_2 (\Omega)$
	V_2	V_1	I_2		
1.	5	2.6	2.1	1.29	4
2.	5	2.57	2.09	1.22	2.39
3.	5	2.62	2.12	1.24	2.35

calculate the

Switch off the

Marks split

Sl

No

1. Exp

2. Obs

3. Ca

4.

5.

Result

& veri

- (Q2) *
- calculate the values of Z parameter using eqn (1) & (2)
 - Switch off the supply after taking the reading

Marks split up:

Sl No	Description	Marks allocated	Marks obtained
1.	Experimental setup	20	20
2.	Observation	20	20
3.	Calculation	20	10
4.	Viva	20	10
5.	Record	20	10
		Total	70

Result $\frac{90}{25/10/25}$

The Z parameters of 2 port network has been calculated & verified using multisim simulator